
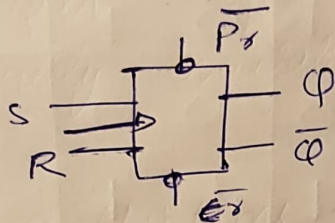
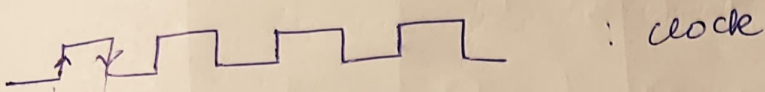


16/10/23


# Sequential circuit : Analysis

Any change in input gets reflected at the output instant.


Combinational + Synchronous = Sequential

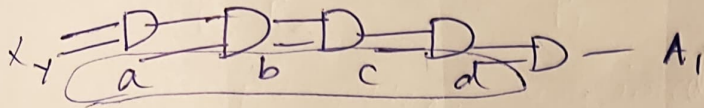


Positive edge trigger SR flip flop

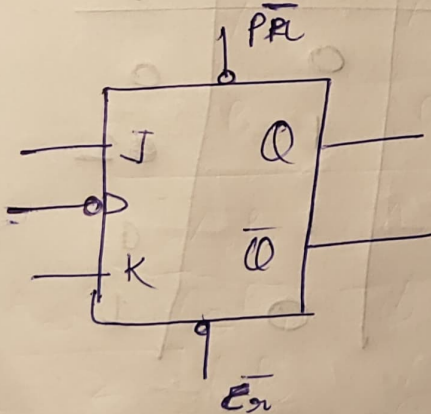

NET JK Flipflop

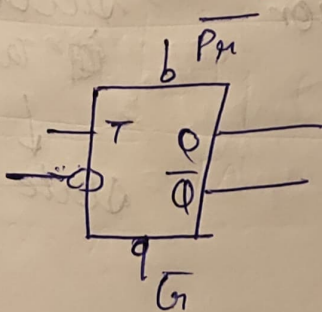

NET T F/F

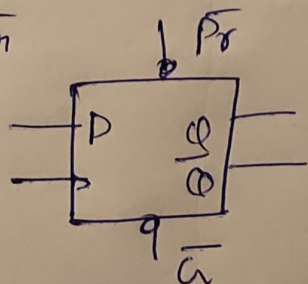

PET D F/F

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	??

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\overline{Q_n}$


T	$Q_{n+1}$
0	$Q_n$
1	$\overline{Q_n}$

D	$Q_{n+1}$
0	0
1	1

Transition table

$Q_n \rightarrow Q_{n+1}$	S R	J K	T	D
0 $\rightarrow$ 0	0 X	0 X	0	0
0 $\rightarrow$ 1	1 0	1 X	1	0
1 $\rightarrow$ 0	0 1	X 1	1	1
1 $\rightarrow$ 1	X 0	X 0	0	1

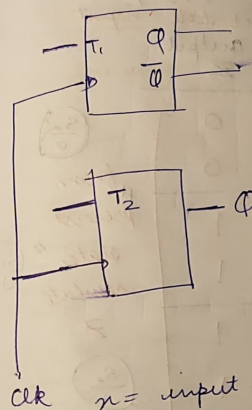
\* Circuit Diagram:- State equation  $\rightarrow$  State Table  
 $\downarrow$   
 State diagram



States

$Q_2$	$Q_1$
0	0
0	1
1	0
1	1

if  $n$  flipflops:  $2^n$  state

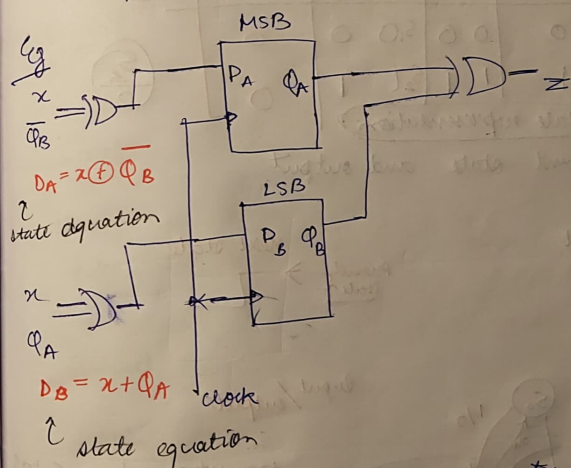

2 flipflops cascaded  $\Rightarrow 2^2 = 4$  states

State table:



Present states		input $x$	input		Next state $Q_A Q_B$	Output $z$
$Q_A$	$Q_B$		$D_A$	$D_B$		
$S_0$	0	0	1	0	$S_2$ 1 0	0
	0	1	0	1	$S_0$ 0 0	0
$S_1$	0	1	1	1	$S_2$ 1 1	1
	1	0	1	0	$S_3$ 1 0	1
$S_2$	1	0	0	1	$S_1$ 0 1	1
	1	1	1	1	$S_2$ 1 1	0
$S_3$	1	1	1	1	$S_2$ 1 1	0

straight binary state representation

State: input, present state and output equation

governs input

State diagram:

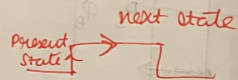
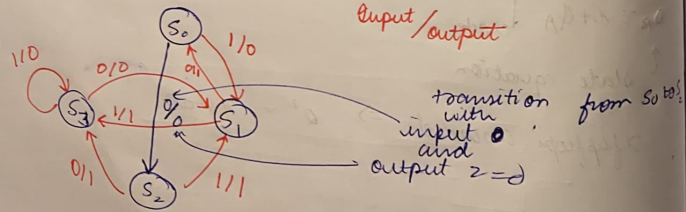


input/output

transition with input and output  $z=0$

Waveform: (wrt clock) "next state"

random input  $x$

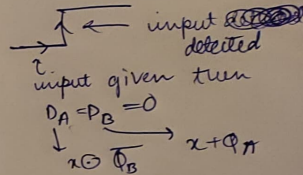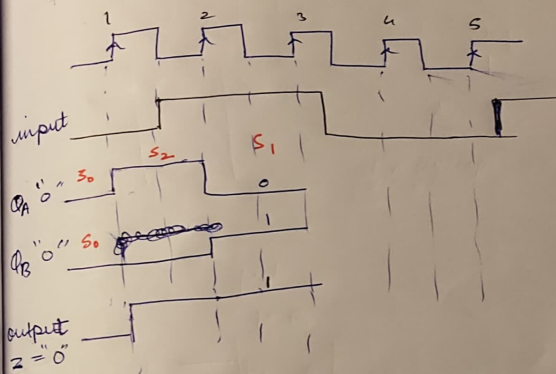

initially  $Q_A, Q_B$  and  $z$  are 0

change in  $Q_A$  and  $Q_B$  will be detected at the edge irrespective of input  $x$  given

Output depends on only state: Moore machine

Mealy machine: